

CONTINUOUS INTERNAL EVALUATION- 1

Dept: FY	Sem / Div: 2 A B C	Sub: Basic Electronics	S Code: 18ELN24
Date: 26.06.2021	Time: 9:30-11:00	Max Marks: 50	Elective: N
Note: Answer any 2 full questions, choosing one full question from each part.			

Q N	Questions	Marks	RBT	COs
PART A				
1 a	Explain the working of PN-junction diode under forward and reverse biased conditions.	9	L2	CO1
b	Explain the working of half-wave rectifier with capacitor filter with neat circuit diagram and wave-forms.	9	L2	CO1
c	A full-wave rectifier uses two diodes having internal resistance of $20\ \Omega$ each. The transformer rms secondary voltage from centre to each end is 50 V. Find V_m , I_m , I_{dc} , V_{dc} and I_{rms} if the load is $980\ \Omega$.	7	L3	CO1
OR				
2 a	What is Zener diode? With neat circuit diagram, explain the operation of Zener diode voltage regulator with and without load?	9	L2	CO1
b	Explain Photo-diode, LED and Photo-coupler. Give minimum two applications of each.	9	L2	CO1
c	A half wave rectifier is fed from a supply of 230 V, 50 Hz with step down transformer of ratio 3:1. Resistive load connected is $2\ k\Omega$. The diode forward resistance is $50\ \Omega$ and transformer secondary is $10\ \Omega$. Calculate the DC load current and DC load voltage.	7	L3	CO1
PART B				
3 a	Explain construction, working and characteristics of N-channel JFET.	9	L2	CO2
b	Explain CMOS as an Inverter with neat circuit diagram. Give its equivalent circuit and its advantages.	9	L3	CO2
c	For a JFET, (i) $I_{DSS} = 9\ mA$ and $V_{GS(off)} = -8\ V$ (max); determine drain current for $V_{GS} = -4\ V$. (ii) $I_{DSS} = 10\ mA$ and drain current 5 mA. If $V_{GS(off)} = -6\ V$; calculate the value of V_{GS} and V_T . (iii) I_{GSS} of $-2\ nA$ for $V_{GS} = -20\ V$. Determine the input resistance.	7	L3	CO2
OR				
4 a	Explain the construction, working and characteristics of N-channel depletion MOSFET.	9	L2	CO2
b	Explain the working of SCR using two-transistor model.	9	L3	CO2
c	For an E-MOSFET, determine the value of I_D , if $I_{D(on)} = 4\ mA$, $V_{GS(on)} = 6\ V$, $V_T = 4\ V$ and $V_{GS} = 8\ V$.	7	L3	CO2